

Relay



Overview

A relay is an electrically-operated switch, often used when a low-power circuit or signal has to control a higher-power circuit. For example, computers like the Raspberry Pi or microcontrollers like found in an Arduino operate in the range of 3.3V/5V DC, where household electrical supply operates at much higher voltages: 110V/220V AC. Using a relay, a lower-powered driver like the Raspberry Pi could control a highered-power circuit like a house light. Originally, relays were used extensively in long-distance telephone systems as amplifiers, with the long-distance system made up of multiple separate circuits arranged end-to-end, each of which “controlled” the next with a relay.

In this experiment, you’ll make your Raspberry operate an electromagnetic relay on one *control circuit* that open and closes a separate *working circuit* on which there is an LED. (In this demonstration, since both circuits are being powered by your Raspberry Pi, they run at similar power levels, and in theory they could all operate as one circuit. However, but in the more general application of relays, the *working circuit* would operate at a higher power level.)

Materials Needed

| | |
|---------------------|----|
| Raspberry Pi | x1 |
| Breadboard | x1 |
| Relay module | x1 |
| LED (3-pin) | x1 |
| Resistor (330Ω) | x1 |
| Dupont jumper wires | |

Experimental Procedure

1. If you have not done so already, prepare your development system by installing the Python interpreter, RPi.GPIO library, and wiringPi library as described in READ_ME_FIRST.TXT.
2. Install the relay and three-pin LED on your breadboard, connecting them with Dupont jumper wires and the resistor to your Raspberry Pi as illustrated in the Wiring Diagram below. Note you will connect only two of the three pins on the LED. Also note that the 3.3V supply simply connects the LED from power, through a resistor and the relay, to ground. Without the relay in the loop, this *working circuit* would create an LED that was **always on**. The +5V *control circuit* controls the relay through pin, and the relay's switch bridges into the *working circuit* to interrupt 3.3V power supply to the LED.
3. Execute the sample stored in this experiment's subfolder.
If using C, compile and execute the C code:


```
cd Code/C
gcc relay.c -o relay.out -lwiringPi
./relay.out
```

If using Python, launch the Python script:

```
cd Code/Python
python relay.py±
```

4. Observe the LED turning on and off on the working circuit as the source code signals the relay on the separate control circuit. Notice that the source code does not control the LED itself; it only controls the relay. As the source code signals the relay on the *control circuit*, the relay switch opens and closes on the working circuit, blinking the LED.

Wiring Diagram

 

Relay pin position:

"S" ↔ Raspberry Pi pin 10

"+" ↔ Raspberry Pi +5V

"-" ↔ Raspberry Pi GND

LED pin position:

"S" ↔ Raspberry Pi +3.3V (through resistor)

"-" ↔ Raspberry Pi GND

Technical Background

- ◆ Operation Voltage: 5V
- ◆ Operation Time: 10ms(max)
- ◆ Insulation Resistance: 100MΩ(min)
- ◆ Ambient Temperature: -25°C~+70°C

◆Ambient Humidity: 45%~85%RH

◆Electrical Level Type: Active High

Sample Code

Python Code

```
#!/usr/bin/env python
import RPi.GPIO as GPIO
import time

RelayPin = 10

def setup():
    GPIO.setmode(GPIO.BOARD)
    GPIO.setup(RelayPin, GPIO.OUT)

def loop():
    while True:
        print '...relayd on'
        GPIO.output(RelayPin, GPIO.HIGH)
        time.sleep(0.5)
        print 'relay off...'
        GPIO.output(RelayPin, GPIO.LOW)
        time.sleep(0.5)

def destroy():
    GPIO.output(RelayPin, GPIO.LOW)
    GPIO.cleanup()           # Release resource

if __name__ == '__main__':    # Program start from here
    setup()
    try:
        loop()
    except KeyboardInterrupt:
        destroy()
```

C Code

```
#include <wiringPi.h>
#include <stdio.h>

#define RelayPin    16

int main(void)
{
    if(wiringPiSetup() == -1)
    {
        printf("setup wiringPi failed !");
        return 1;
    }

    pinMode(RelayPin, OUTPUT);
    while(1)
    {
        digitalWrite(RelayPin, HIGH);
        delay(500);
        digitalWrite(RelayPin, LOW);
        delay(500);
    }

    return 0;
}
```